

Off-Campus Centre of Nitte (Deemed to be University)
I Sem B.Tech. (CBCS) Mid Semester Examinations - I, September 2022
EE1001-1 – BASIC ELECTRICAL ENGINEERING


Duration: 1 Hour

Max. Marks: 20

Note: Answer any One full question from each Unit.

Unit – I

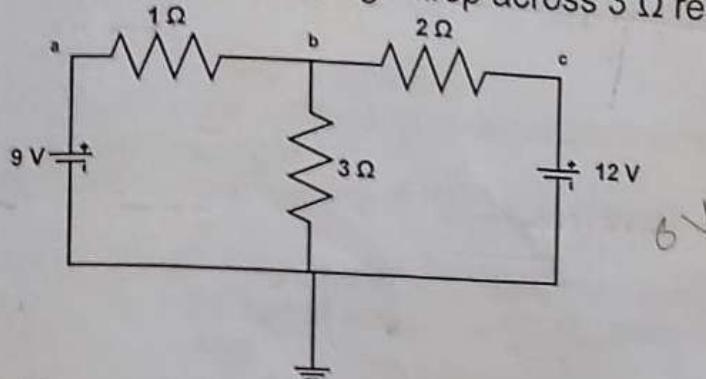1. a) Using mesh analysis, find voltage drop across $3\ \Omega$ resistor.




Marks BT* CO* PO*

- b) Define (i) Power Factor (ii) form factor (iii) peak factor (iv) frequency (v) phase.

5 L*1 1 1,2

5 L1 1 1,2

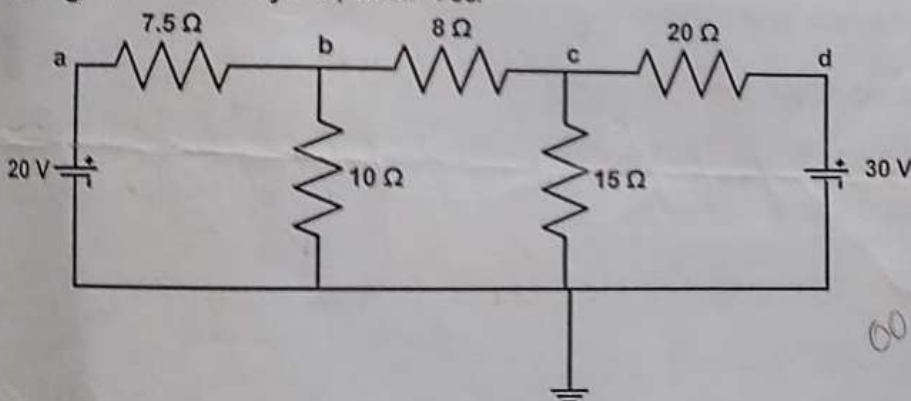2. a) Using Nodal analysis, find V_{bc} .



5 L1 1 1,2

- b) Define RMS value of an alternating quantity and derive the expression for the same.

5 L1 1 1,2

Unit – II

3. a) Show that the power consumed in pure inductance circuit is zero. Draw the current, voltage and power waveform.
 b) A $318\ \mu\text{F}$ capacitor is connected across a $230\ \text{V}$, $50\ \text{Hz}$ system. Find (i) the capacitive reactance (ii) RMS value of current and (iii) equations for voltage and current.

5 L1 2 1,2

5 L1 2 1,2

4. a) Show that the power consumed in pure capacitance circuit is zero. Draw the current, voltage and power waveform.

5 L1 2 1,2

- b) A coil having a resistance of $10\ \Omega$ and an inductance of $35\ \text{mH}$ is connected to $230\ \text{V}$, $50\ \text{Hz}$ supply. Calculate (i) the impedance and the circuit current (ii) phase angle (iii) power factor (iv) power consumed.

5 L1 2 1,2

BT* Bloom's Taxonomy, L* Level; CO* Course Outcome; PO* Program Outcome
