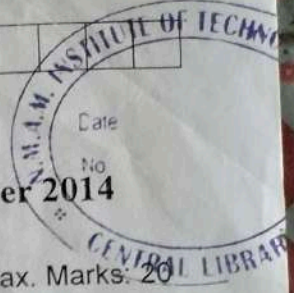


Sections

USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--



NMAM INSTITUTE OF TECHNOLOGY, NITTE
(An Autonomous Institution affiliated to VTU, Belgaum)
I Sem B.E. (Credit System) Mid Semester Examinations – I, September 2014

Duration: 1 Hour

14EE105 – BASIC ELECTRICAL ENGINEERING

Max. Marks: 20

Note: Answer any **One** full question from **each Unit**.

Unit – I

1. a) With an example explain Kirchoff's Laws. 4
b) The two coils A and B placed in a parallel plane having inductances 6H and 0.06H respectively with a coefficient of coupling $K=0.9$. Find the emf induced in both coils when the current in coil A increases at the rate of 100A/Second. 6
2. a) Find the equivalent resistance between terminals A and B of the circuit shown in Fig. 2(a). 6

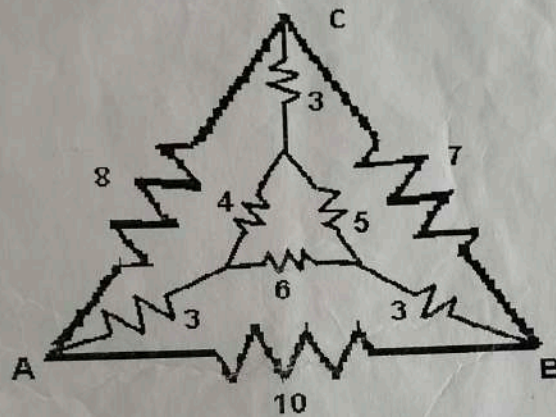


Fig. 2(a)

- b) State and Illustrate Faraday's Laws of electromagnetic Induction and lenz's law. 4

Unit – II

3. a) Prove that power consumed by a pure inductance is zero 4
b) A coil having a resistance of 10 Ω and an inductance of 35mH is connected to 230V, 50Hz supply. Calculate (i) the circuit current (ii) phase angle (iii) power factor (iv) power consumed. Draw phasor diagram. 6
4. a) State the definition of RMS value, Average value, Form factor, Peak Factor. 4
b) A series circuit having pure resistance of 40 Ω , pure inductance of 50.07mH and a capacitor connected across 400V, 50Hz AC supply. This R,L,C combination draws a current of 10A. Calculate i) Capacitance value ii) Power factor.
